

PWM Inverters

Rijil Ramchand
Associate Professor
NIT Calicut

Inverters

Classifications

- Single phase & three phase
- Voltage Source & Current source
- Two-level & Multi-level

Voltage Source Inverter

Topics


- Sinusoidal PWM
- Space vector modulation

Why Use PWM Techniques?


- To control inverter output frequency (fundamental)
- To control inverter output voltage (fundamental)
- To minimize harmonic distortion

Voltage Source Inverter

Open loop voltage control

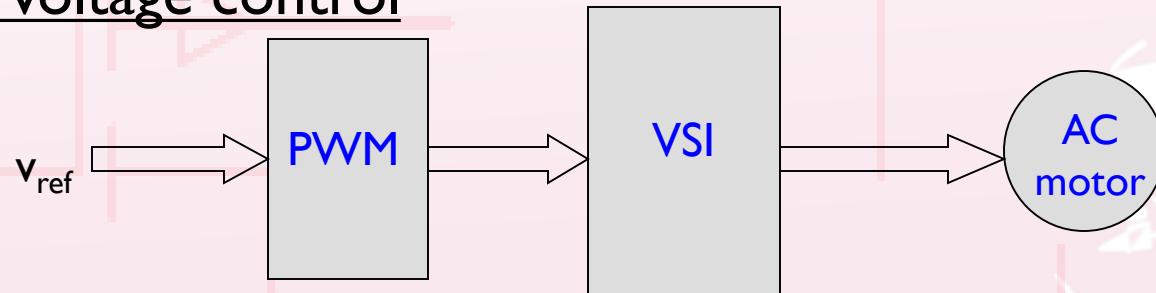


Closed loop current-control

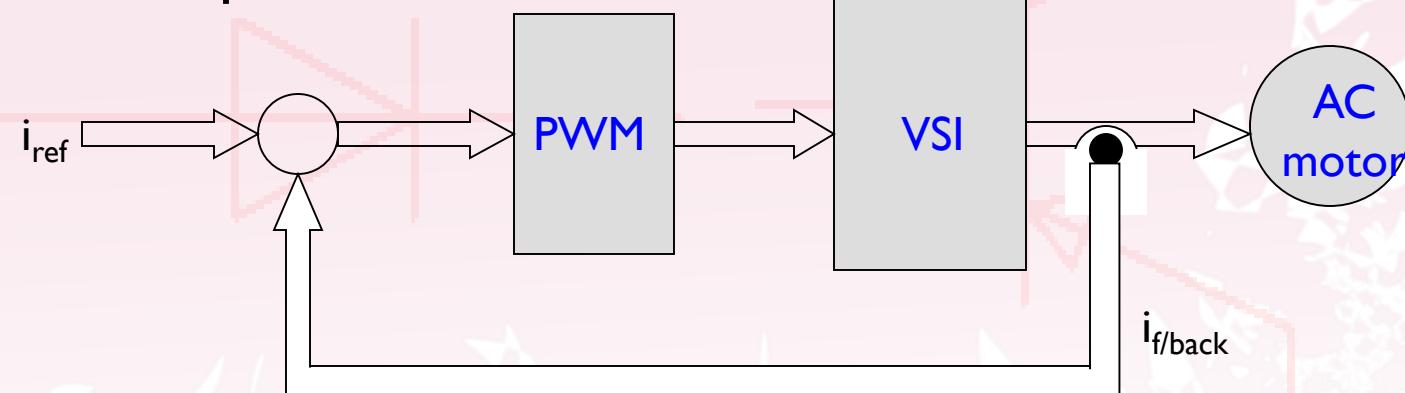

Voltage Source Inverter


Inverter Configuration

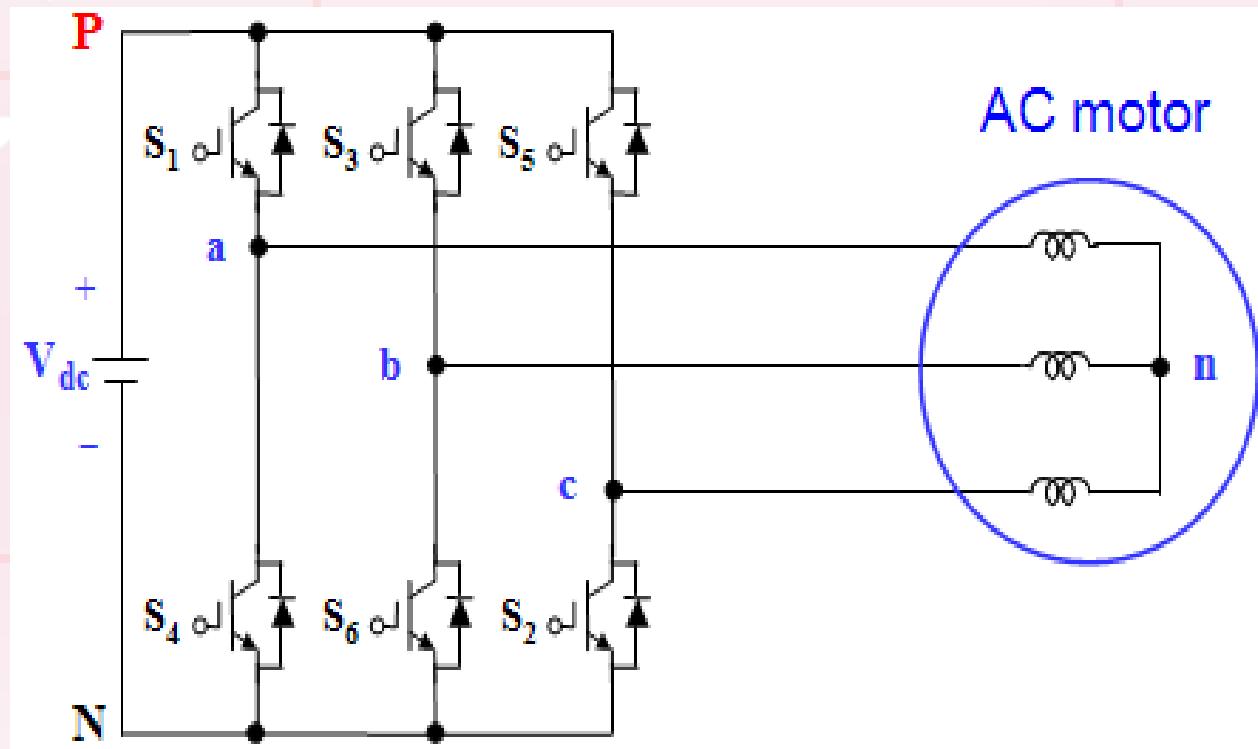

Voltage Source Inverter (VSI)

Six-Step VSI

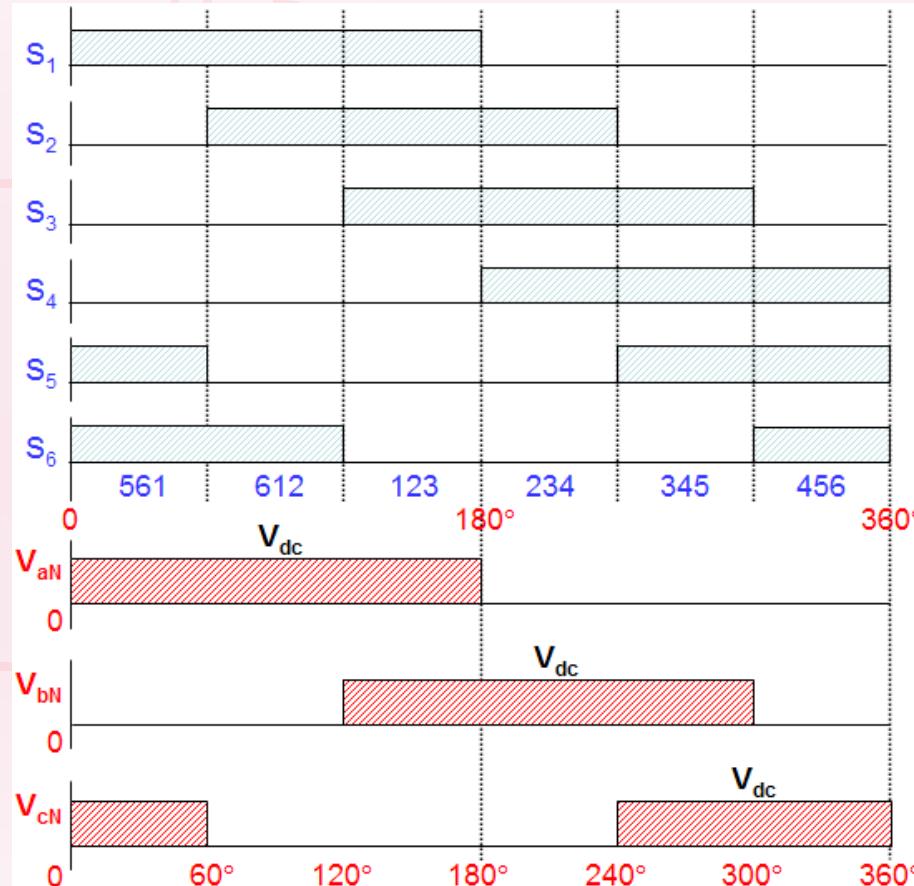- Gating signals, switching sequence and line to negative voltages



Waveforms of gating signals, switching sequence, line to negative voltages for six-step voltage source inverter.







Voltage Source Inverter (VSI)

Six-Step VSI

➤ Switching Sequence:

561 (V_1) → 612 (V_2) → 123 (V_3) → 234 (V_4) → 345 (V_5) → 456 (V_6) → 561 (V_1)

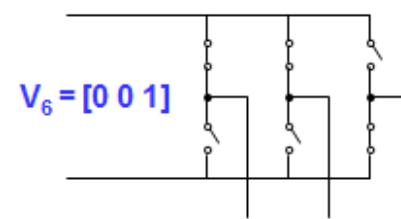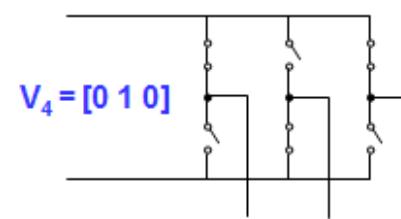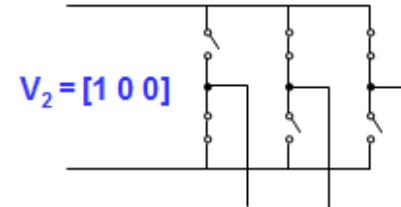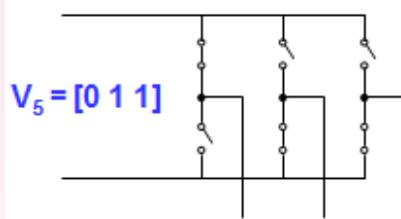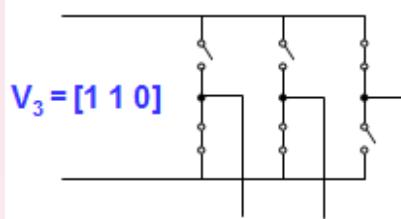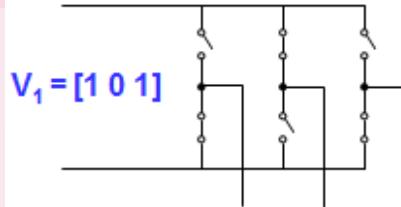where, 561 means that S_5 , S_6 and S_1 are switched on



Six inverter voltage vectors for six-step voltage source inverter.

Voltage Source Inverter (VSI)

Six-Step VSI

➤ Line to line voltages (V_{ab} , V_{bc} , V_{ca}) and line to neutral voltages (V_{an} , V_{bn} , V_{cn})

♦ Line to line voltages

$$\Rightarrow V_{ab} = V_{aN} - V_{bN}$$

$$\Rightarrow V_{bc} = V_{bN} - V_{cN}$$


$$\Rightarrow V_{ca} = V_{cN} - V_{aN}$$

♦ Phase voltages

$$\Rightarrow V_{an} = \frac{2}{3}V_{aN} - \frac{1}{3}V_{bN} - \frac{1}{3}V_{cN}$$

$$\Rightarrow V_{bn} = -\frac{1}{3}V_{aN} + \frac{2}{3}V_{bN} - \frac{1}{3}V_{cN}$$

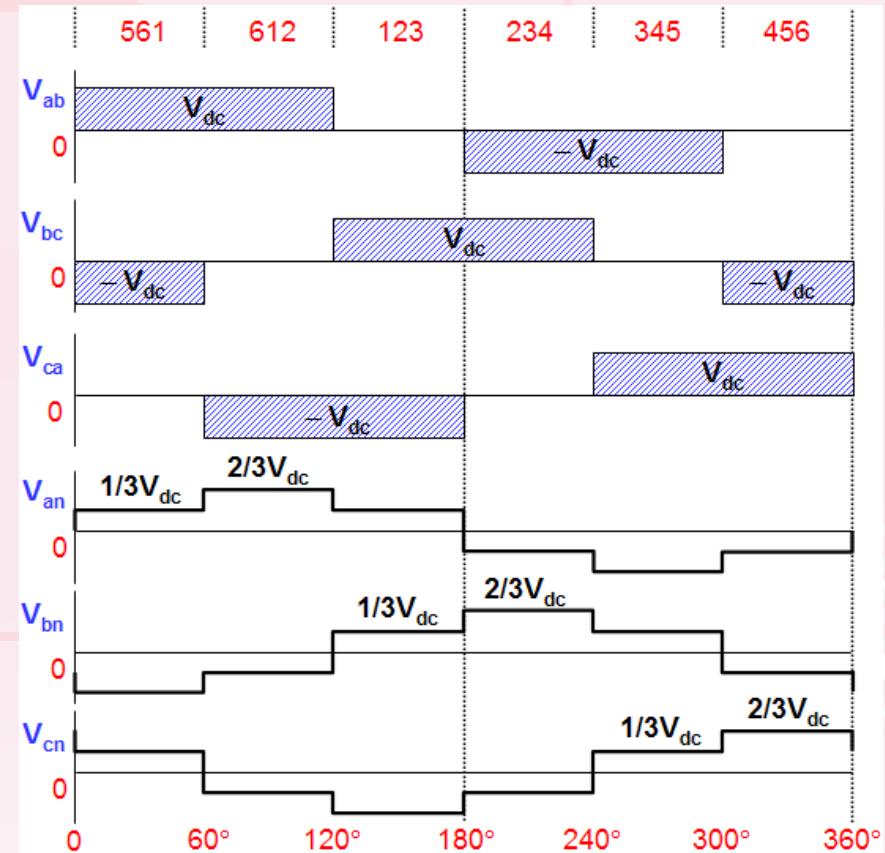
$$\Rightarrow V_{cn} = -\frac{1}{3}V_{aN} - \frac{1}{3}V_{bN} + \frac{2}{3}V_{cN}$$



Waveforms of line to neutral (phase) voltages and line to line voltages
for six-step voltage source inverter.

Voltage Source Inverter (VSI)

Six-Step VSI

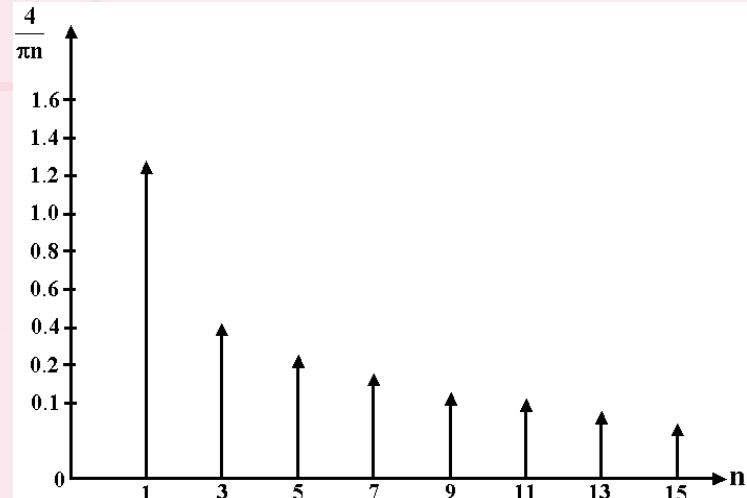

Harmonic spectrum of a square wave

Voltage Source Inverter (VSI)

Six-Step VSI

- Amplitude of line to line voltages (V_{ab} , V_{bc} , V_{ca})

- Fundamental Frequency Component (V_{ab})₁

$$(V_{ab})_1(\text{rms}) = \frac{\sqrt{3}}{\sqrt{2}} \frac{4}{\pi} \frac{V_{dc}}{2} = \frac{\sqrt{6}}{\pi} V_{dc} \approx 0.78 V_{dc}$$

- Harmonic Frequency Components (V_{ab})_h

: amplitudes of harmonics decrease inversely proportional to their harmonic order

$$(V_{ab})_h(\text{rms}) = \frac{0.78}{h} V_{dc}$$

where, $h = 6n \pm 1$ ($n = 1, 2, 3, \dots$)

Voltage Source Inverter (VSI)


Six-Step VSI

➤ Characteristics of Six-step VSI

- ♦ It is called “six-step inverter” because of the presence of six “steps” in the line to neutral (phase) voltage waveform
- ♦ Harmonics of order three and multiples of three are absent from both the line to line and the line to neutral voltages and consequently absent from the currents
- ♦ Output amplitude in a three-phase inverter can be controlled by only change of DC-link voltage (V_{dc})

Sinusoidal PWM

Modulating and Carrier Waves

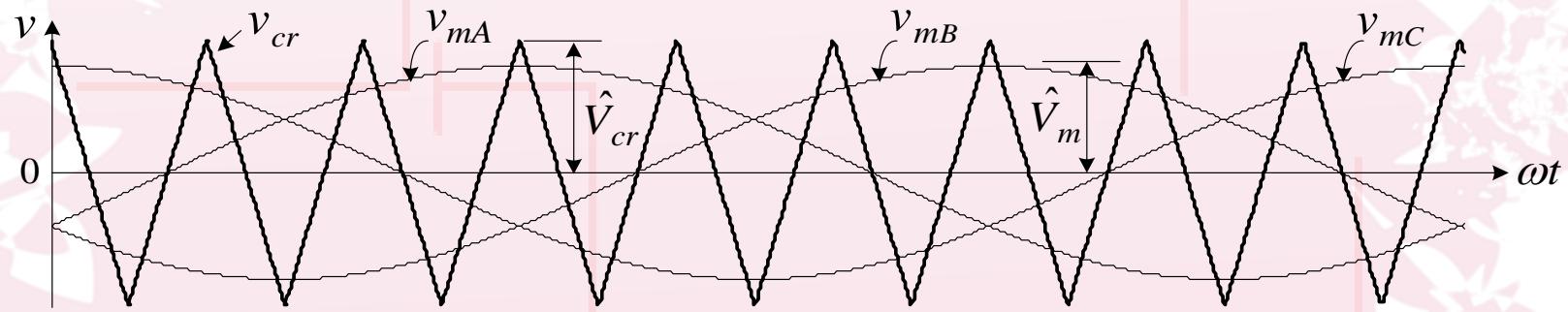

- V_{cr} – Carrier wave (triangle)

- Amplitude modulation index

$$m_a = \frac{\hat{V}_m}{\hat{V}_{cr}}$$

- V_m – Modulating wave (sine)

- Frequency modulation index


$$m_f = \frac{f_{cr}}{f_m}$$

Sinusoidal PWM

- ♦ **m_f should be an odd integer**
 - ⇒ if m_f is not an integer, there may exist sub-harmonics at output voltage
 - ⇒ if m_f is not odd, DC component may exist and even harmonics are present at output voltage
- ♦ **m_f should be a multiple of 3 for three-phase PWM inverter**
 - ⇒ An odd multiple of 3 and even harmonics are suppressed

Sinusoidal PWM



Gate Signal Generation

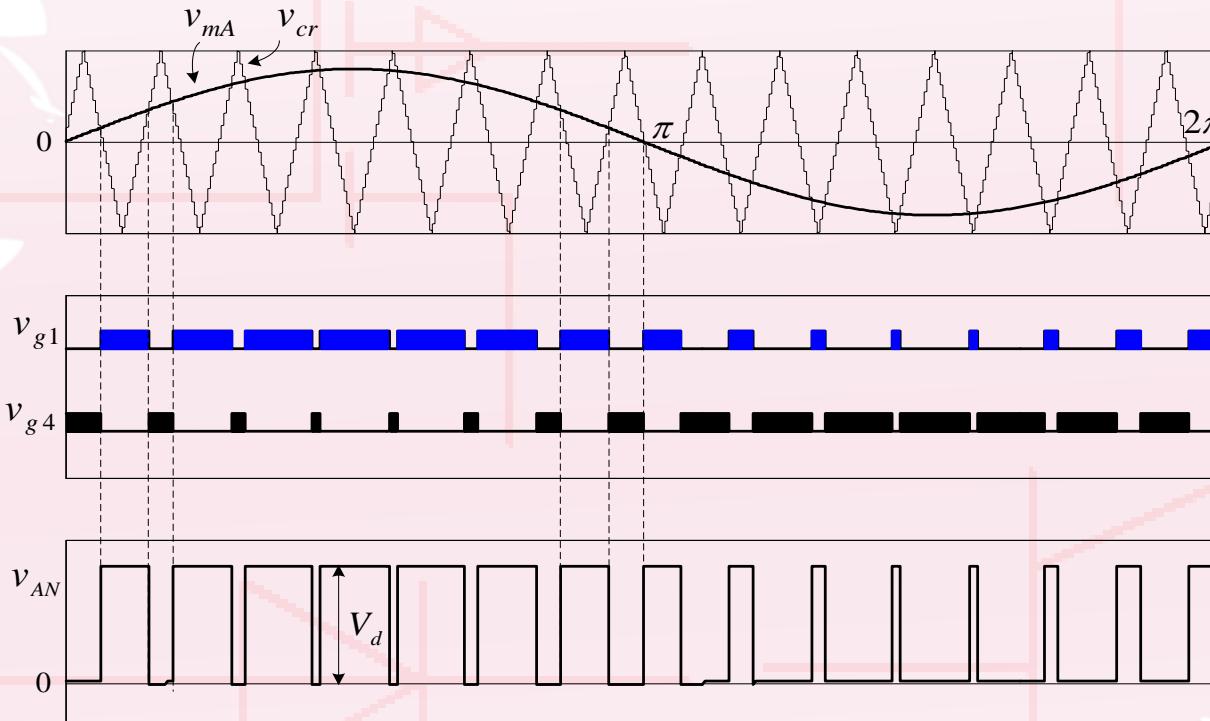

Phase A	$v_{mA} > v_{cr}$	$v_{g1} > 0 \quad (v_{g4} < 0)$	S_1 on (S_4 off)	$v_{AN} = V_d$
	$v_{mA} < v_{cr}$	$v_{g4} > 0 \quad (v_{g1} < 0)$	S_4 on (S_1 off)	$v_{AN} = 0$





Sinusoidal PWM

Line-to-Line Voltage v_{AB}

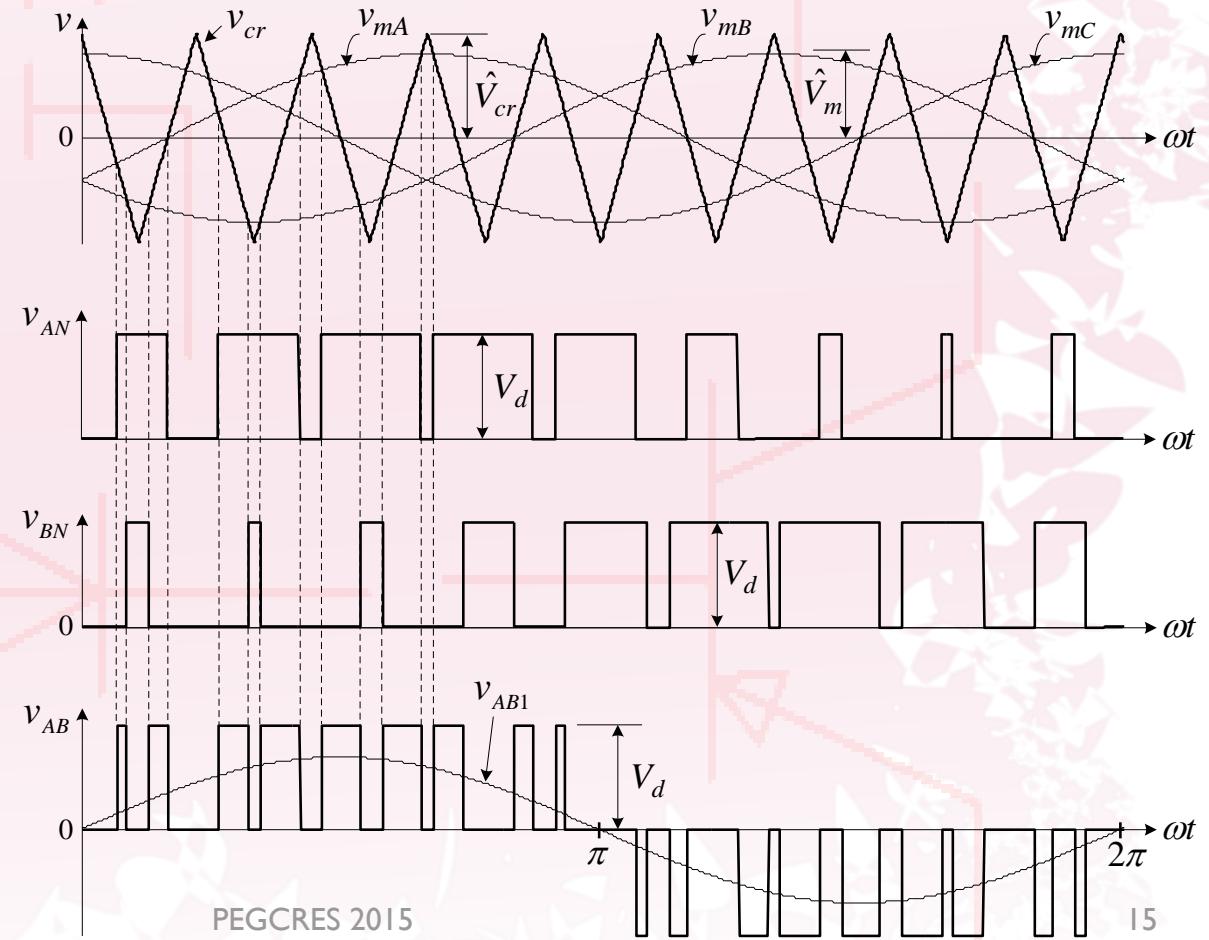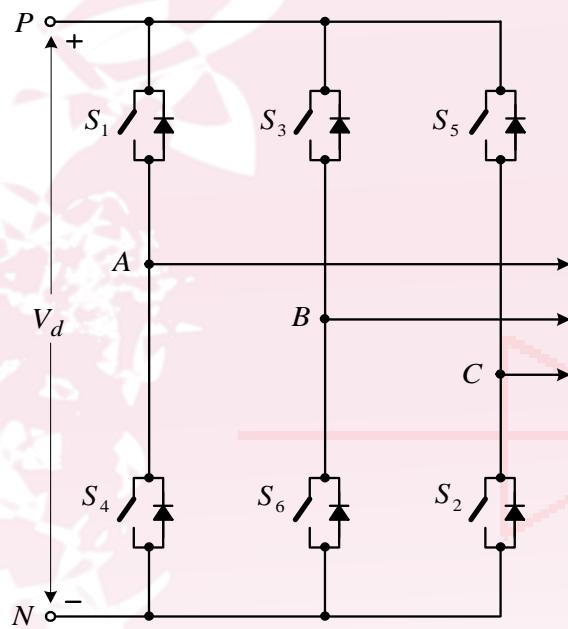

Sinusoidal PWM

Waveforms and FFT

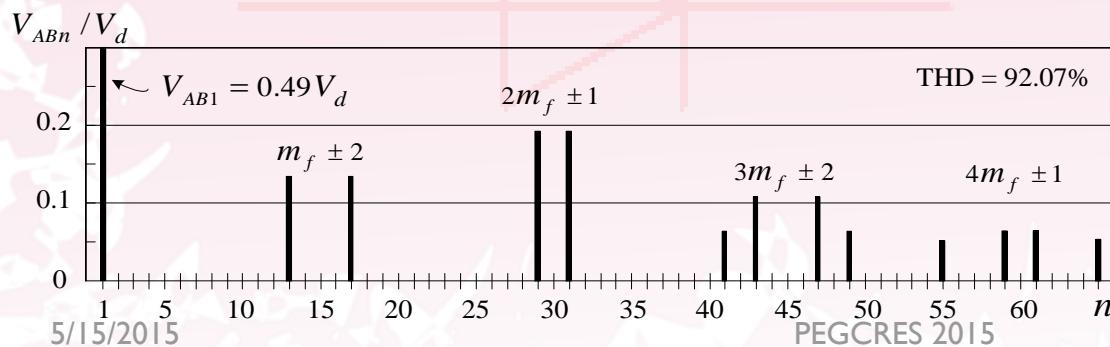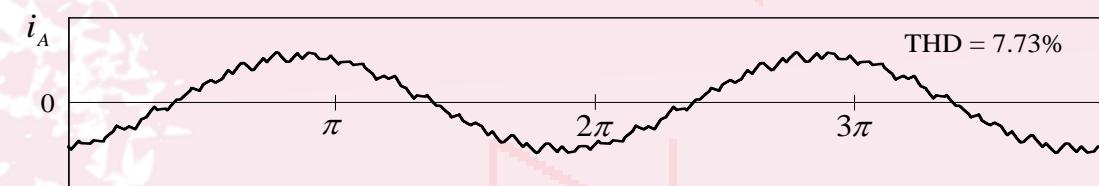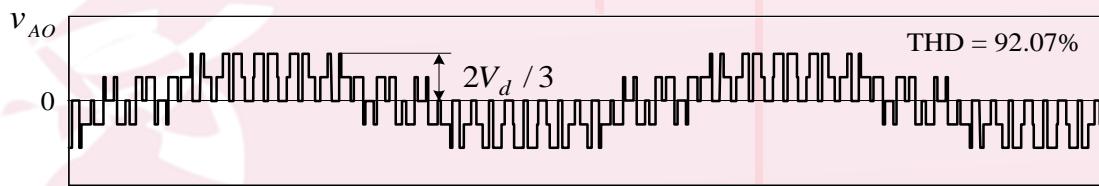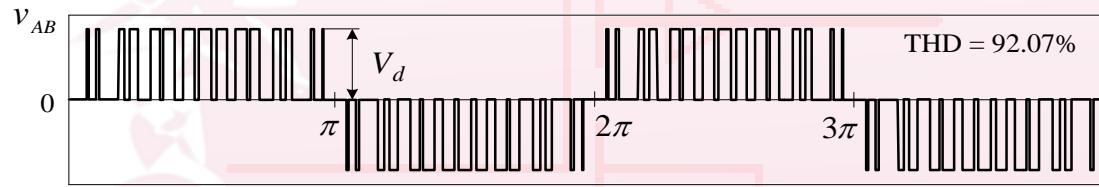


$m_a = 0.8$, $m_f = 15$,
 $f_m = 60\text{Hz}$, $f_{cr} = 900\text{Hz}$

Switching frequency
 $f_{sw} = f_{cr} = 900\text{Hz}$



Sinusoidal PWM

Over-Modulation

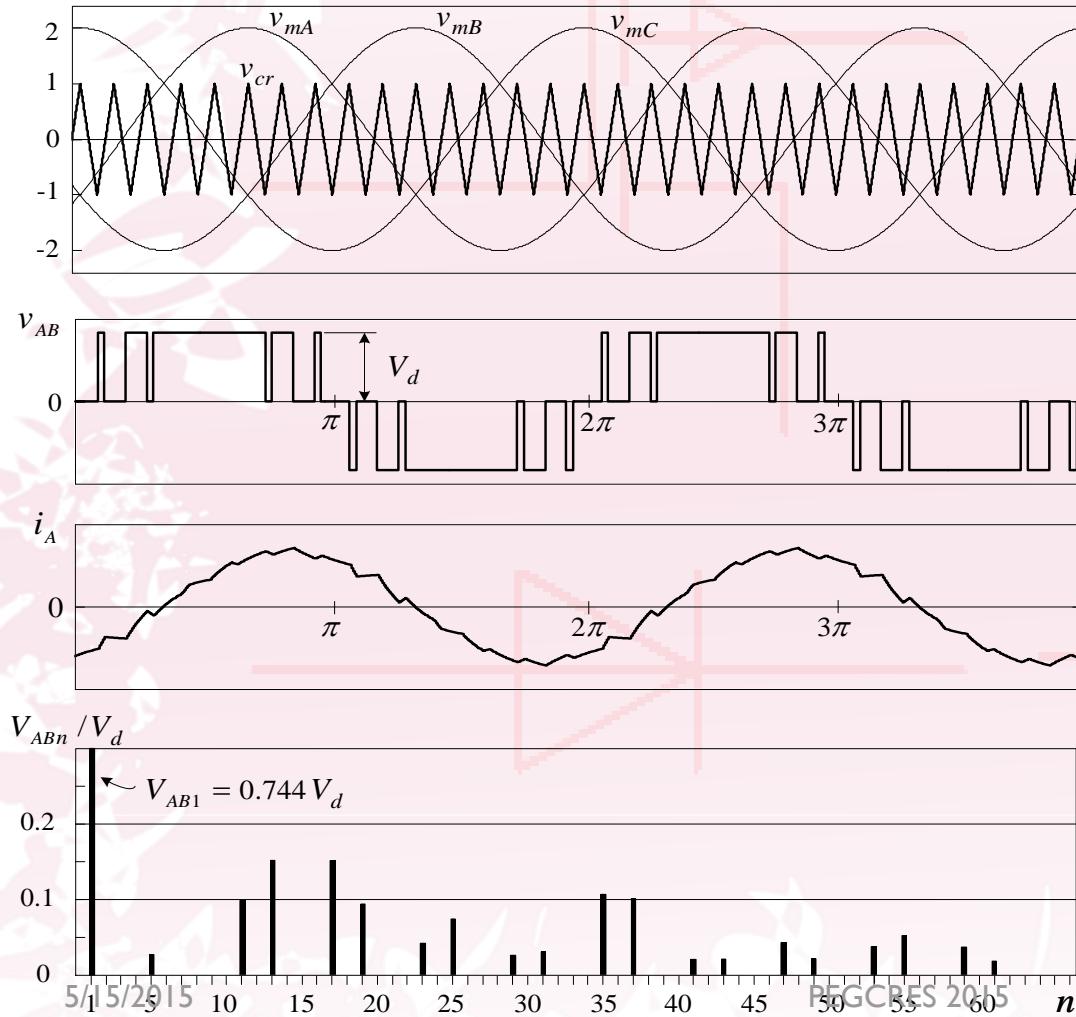

Fundamental voltage ↑
Low-order harmonics ↑

Sinusoidal PWM

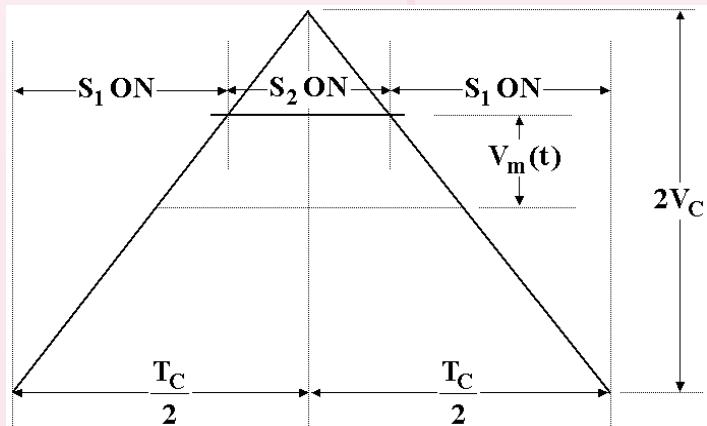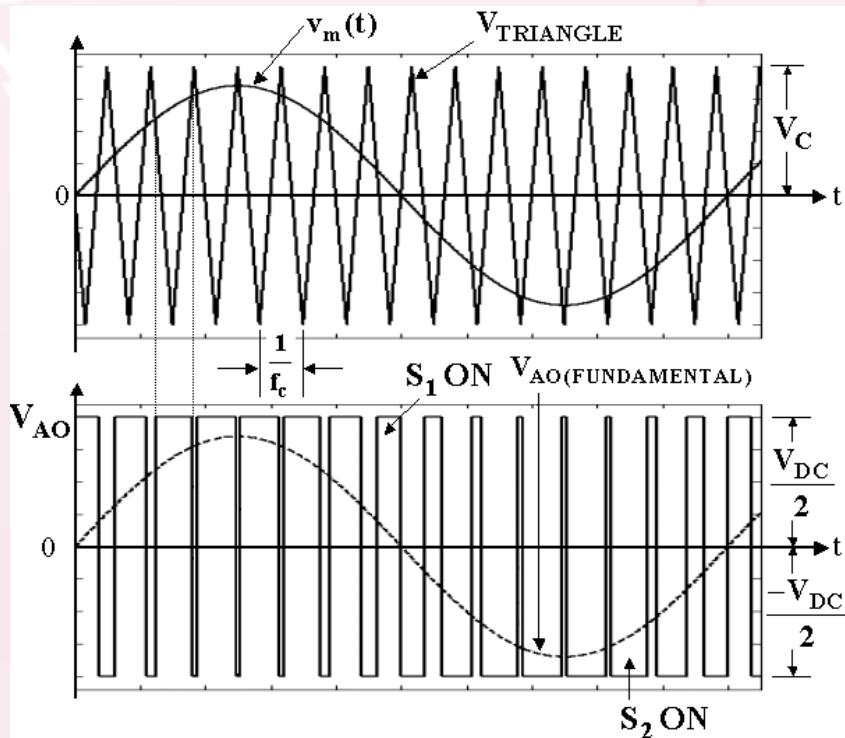


$$S_1 \text{ ON period} = 2 \frac{T_c}{2} \left(\frac{V_c + v_m(t)}{2V_c} \right) \rightarrow V_{AO} \text{ is } V_{DC}/2$$

$$S_2 \text{ ON period} = T_c - T_c \left(\frac{V_c + v_m(t)}{2V_c} \right) \rightarrow V_{AO} \text{ is } -V_{DC}/2$$

$$\begin{aligned} V_{AO} \text{ average for a period } T_c &= \frac{1}{T_c} \left(\frac{T_c}{2} + \frac{T_c v_m(t)}{2V_c} - \frac{T_c}{2} + \frac{T_c v_m(t)}{2V_c} \right) \frac{V_{DC}}{2} \\ &= \frac{V_{DC}}{2} \frac{v_m(t)}{V_c} \end{aligned}$$

Space Vector Modulation


Switching States (Three-Phase)

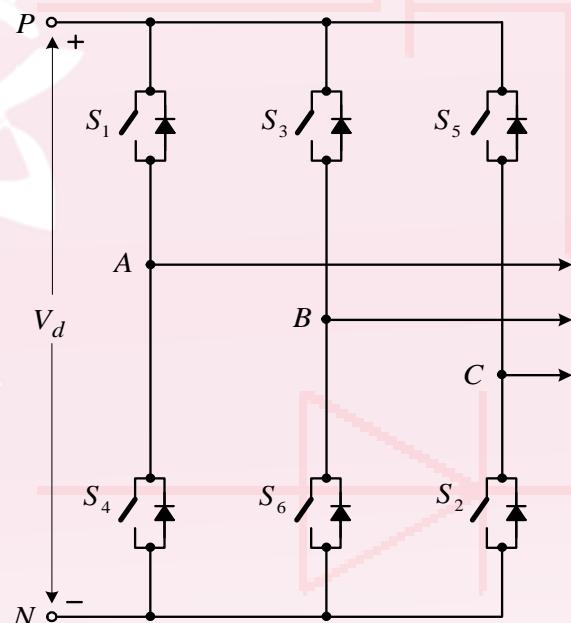

Switching State (Three Phases)	On-state Switch
[PPP]	S ₁ , S ₃ , S ₅
[OOO]	S ₄ , S ₆ , S ₂
[POO]	S ₁ , S ₆ , S ₂
[PPO]	S ₁ , S ₃ , S ₂
[OPO]	S ₄ , S ₃ , S ₂
[OPP]	S ₄ , S ₃ , S ₅
[OOP]	S ₄ , S ₆ , S ₅
[POP]	S ₁ , S ₆ , S ₅

Space Vector Modulation

Space Vector Diagram

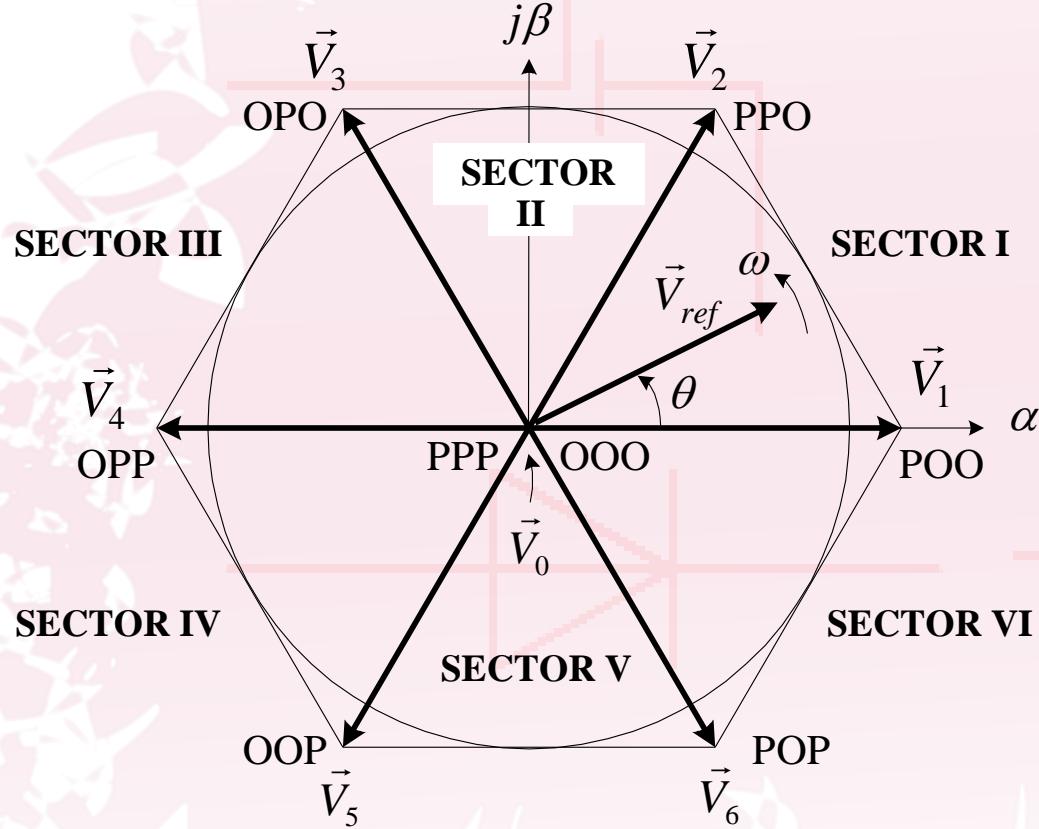

Active vectors: \vec{V}_1 to \vec{V}_6
(stationary, not rotating)

Zero vector: \vec{V}_0

Six sectors: I to VI

Space Vector Modulation

Space Vectors

Three-phase voltages

$$v_{AO}(t) + v_{BO}(t) + v_{CO}(t) = 0 \quad (1)$$

Two-phase voltages

$$\begin{bmatrix} v_\alpha(t) \\ v_\beta(t) \end{bmatrix} = \frac{2}{3} \begin{bmatrix} \cos 0 & \cos \frac{2\pi}{3} & \cos \frac{4\pi}{3} \\ \sin 0 & \sin \frac{2\pi}{3} & \sin \frac{4\pi}{3} \end{bmatrix} \begin{bmatrix} v_{AO}(t) \\ v_{BO}(t) \\ v_{CO}(t) \end{bmatrix} \quad (2)$$

Space vector representation

$$\vec{V}(t) = v_\alpha(t) + j v_\beta(t) \quad (3)$$

(2) → (3)

$$\vec{V}(t) = \frac{2}{3} [v_{AO}(t)e^{j0} + v_{BO}(t)e^{j2\pi/3} + v_{CO}(t)e^{j4\pi/3}] \quad (4)$$

where $e^{jx} = \cos x + j \sin x$

Space Vector Modulation

Space Vectors (Example)

Switching state [POO] → S_1 , S_6 and S_2 ON


$$v_{AO}(t) = \frac{2}{3}V_d, v_{BO}(t) = -\frac{1}{3}V_d, v_{CO}(t) = -\frac{1}{3}V_d$$

(5) → (4)

$$\vec{V}_1 = \frac{2}{3}V_d e^{j0}$$


$$\vec{V}_k = \frac{2}{3}V_d e^{j(k-1)\frac{\pi}{3}}$$

$$k = 1, 2, \dots, 6.$$

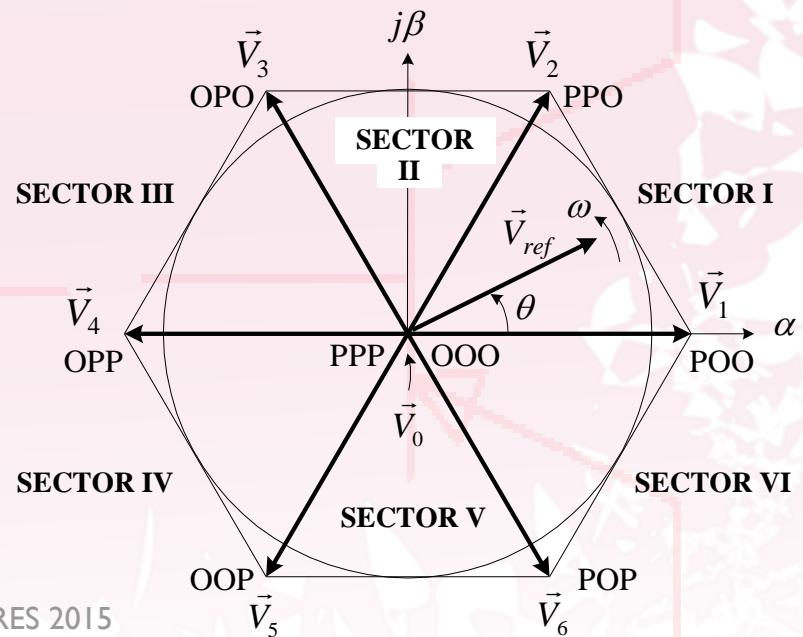

Space Vector Modulation

Active and Zero Vectors

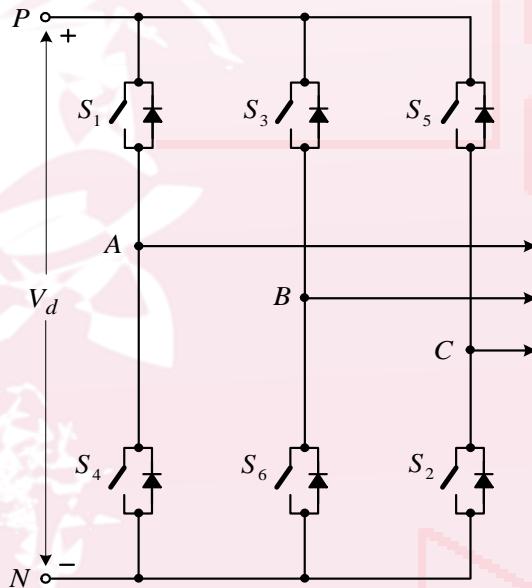

Active Vector: 6

Zero Vector: 1

Redundant switching states: [PPP] and [OOO]

5/15/2015

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	\vec{V}_0	[PPP]	S_1, S_3, S_5	$\vec{V}_0 = 0$
		[OOO]	S_4, S_6, S_2	
Active Vector	\vec{V}_1	[POO]	S_1, S_6, S_2	$\vec{V}_1 = \frac{2}{3}V_d e^{j0}$
	\vec{V}_2	[PPO]	S_1, S_3, S_2	$\vec{V}_2 = \frac{2}{3}V_d e^{j\frac{\pi}{3}}$
	V_3	[OPO]	S_4, S_3, S_2	$\vec{V}_3 = \frac{2}{3}V_d e^{j\frac{2\pi}{3}}$
	V_4	[OPP]	S_4, S_3, S_5	$\vec{V}_4 = \frac{2}{3}V_d e^{j\frac{3\pi}{3}}$
	\vec{V}_5	[OOP]	S_4, S_6, S_5	$\vec{V}_5 = \frac{2}{3}V_d e^{j\frac{4\pi}{3}}$
	\vec{V}_6	[POP]	S_1, S_6, S_5	$\vec{V}_6 = \frac{2}{3}V_d e^{j\frac{5\pi}{3}}$
	PEGCRES 2015			23

Space Vector Modulation

Definition

$$\vec{V}_{ref} = V_{ref} e^{j\theta}$$


Rotating in space at ω

$$\omega = 2\pi f \quad (8)$$

Angular displacement

$$\theta(t) = \int_0^t \omega dt \quad (9)$$

Reference Vector V_{ref}

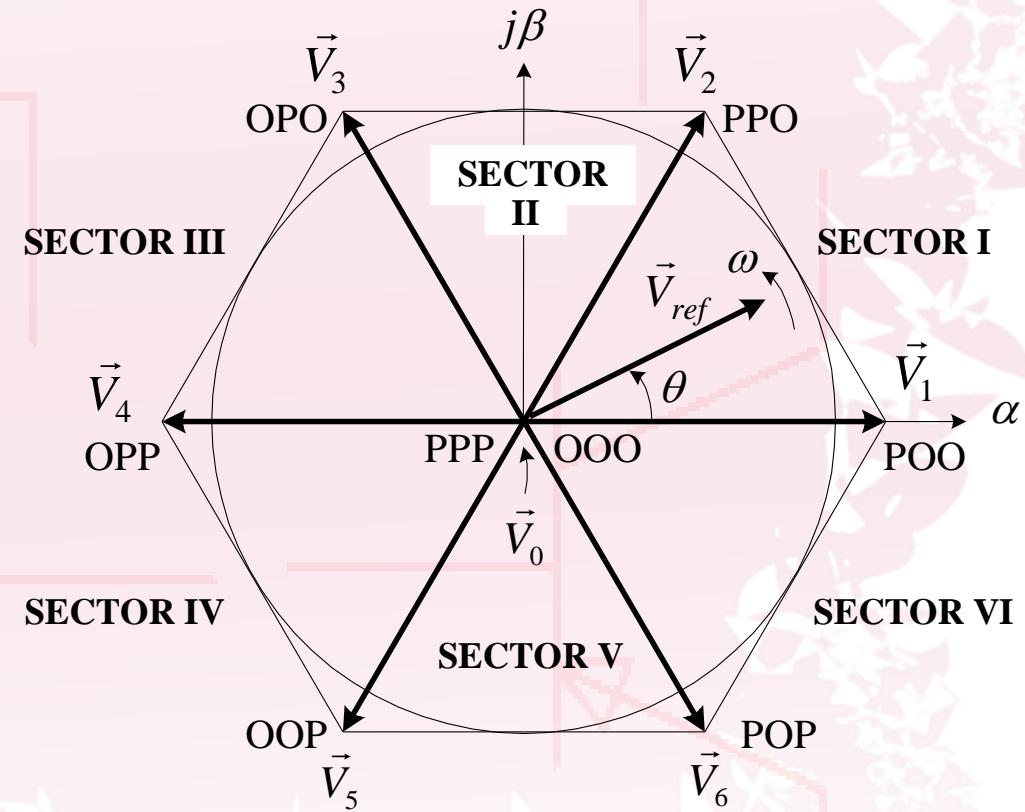


Space Vector Modulation

Relationship Between V_{ref} and V_{AB}

V_{ref} is approximated by two active and zero vectors

V_{ref} rotates one revolution,
 V_{AB} completes one cycle

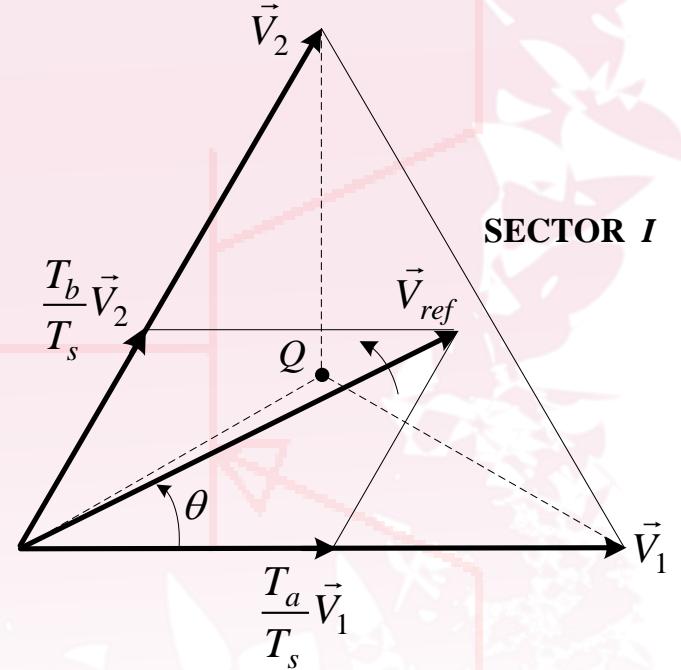Length of V_{ref} corresponds to magnitude of V_{AB}



Space Vector Modulation

Dwell Time Calculation

Volt-Second Balancing

$$\begin{cases} \vec{V}_{ref} T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases} \quad (10)$$

T_a , T_b and T_0 – dwell times for \vec{V}_1 , \vec{V}_2 and \vec{V}_0


T_s – sampling period

Space vectors

$$\vec{V}_{ref} = V_{ref} e^{j\theta}, \vec{V}_1 = \frac{2}{3} \vec{V}_d, \vec{V}_2 = \frac{2}{3} \vec{V}_d e^{j\frac{\pi}{3}} \quad \text{and} \quad \vec{V}_0 = 0 \quad (11)$$

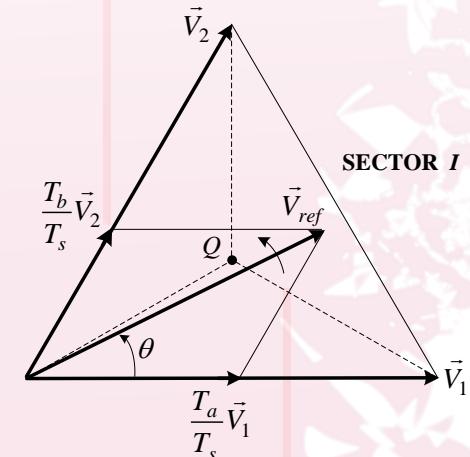(11) \rightarrow (10)

$$\begin{cases} \text{Re : } V_{ref} (\cos \theta) T_s = \frac{2}{3} V_d T_a + \frac{1}{3} V_d T_b \\ \text{Im : } V_{ref} (\sin \theta) T_s = \frac{1}{\sqrt{3}} V_d T_b \end{cases} \quad (12)$$



Space Vector Modulation


Dwell Times

Solve (12)

$$\begin{cases} T_a = \frac{\sqrt{3}T_s V_{ref}}{V_d} \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = \frac{\sqrt{3}T_s V_{ref}}{V_d} \sin \theta \\ T_0 = T_s - T_a - T_b \end{cases} \quad 0 \leq \theta < \pi/3 \quad (13)$$

Space Vector Modulation

V_{ref} Location versus Dwell Times

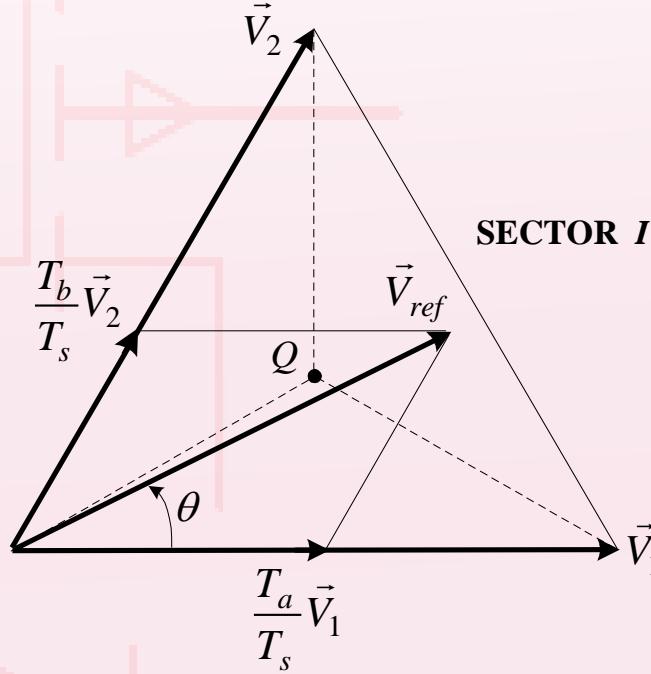

\vec{V}_{ref} Location	$\theta = 0$	$0 < \theta < \frac{\pi}{6}$	$\theta = \frac{\pi}{6}$	$\frac{\pi}{6} < \theta < \frac{\pi}{3}$	$\theta = \frac{\pi}{3}$
Dwell Times	$T_a > 0$ $T_b = 0$	$T_a > T_b$	$T_a = T_b$	$T_a < T_b$	$T_a = 0$ $T_b > 0$

Space Vector Modulation

Modulation Index

$$\begin{cases} T_a = T_s m_a \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = T_s m_a \sin\theta \\ T_0 = T_s - T_b - T_c \end{cases}$$

(15)

$$m_a = \frac{\sqrt{3} V_{ref}}{V_d}$$

(16)

Space Vector Modulation

Modulation Range


$V_{ref,max}$

$$V_{ref,max} = \frac{2}{3} V_d \times \frac{\sqrt{3}}{2} = \frac{V_d}{\sqrt{3}} \quad (17)$$

(17) \rightarrow (16)


$m_{a,max} = 1 \rightarrow$

Modulation range: $0 \leq m_a \leq 1$

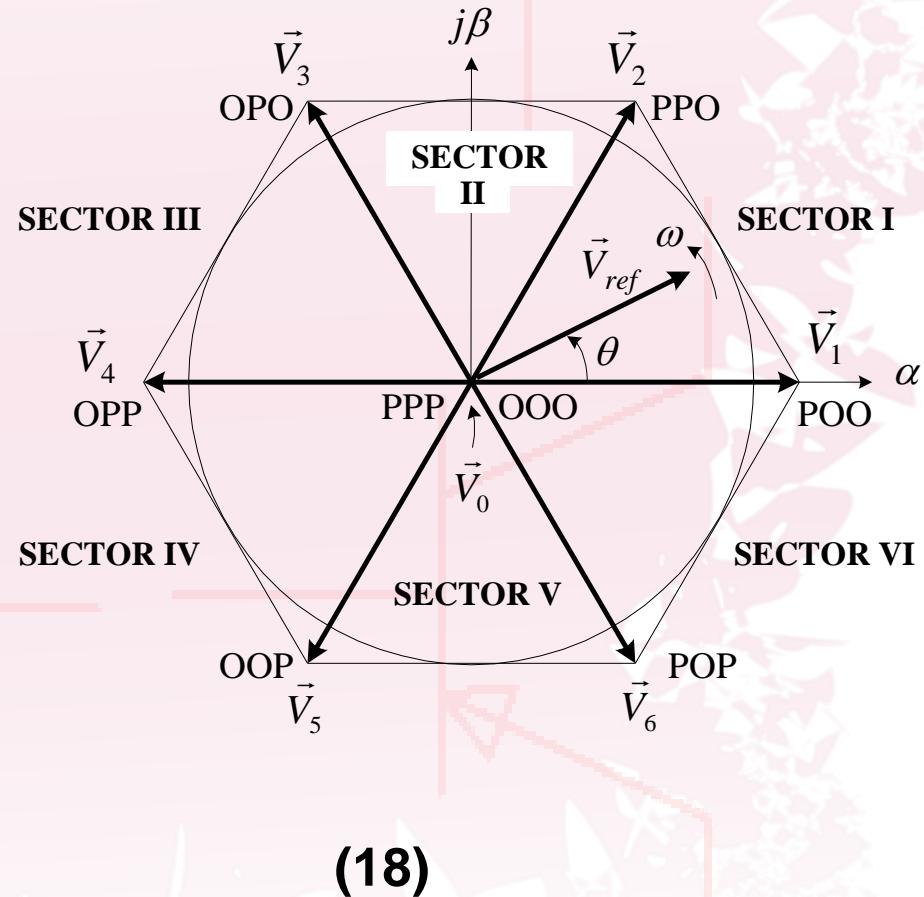





Space Vector Modulation

Simulated Waveforms


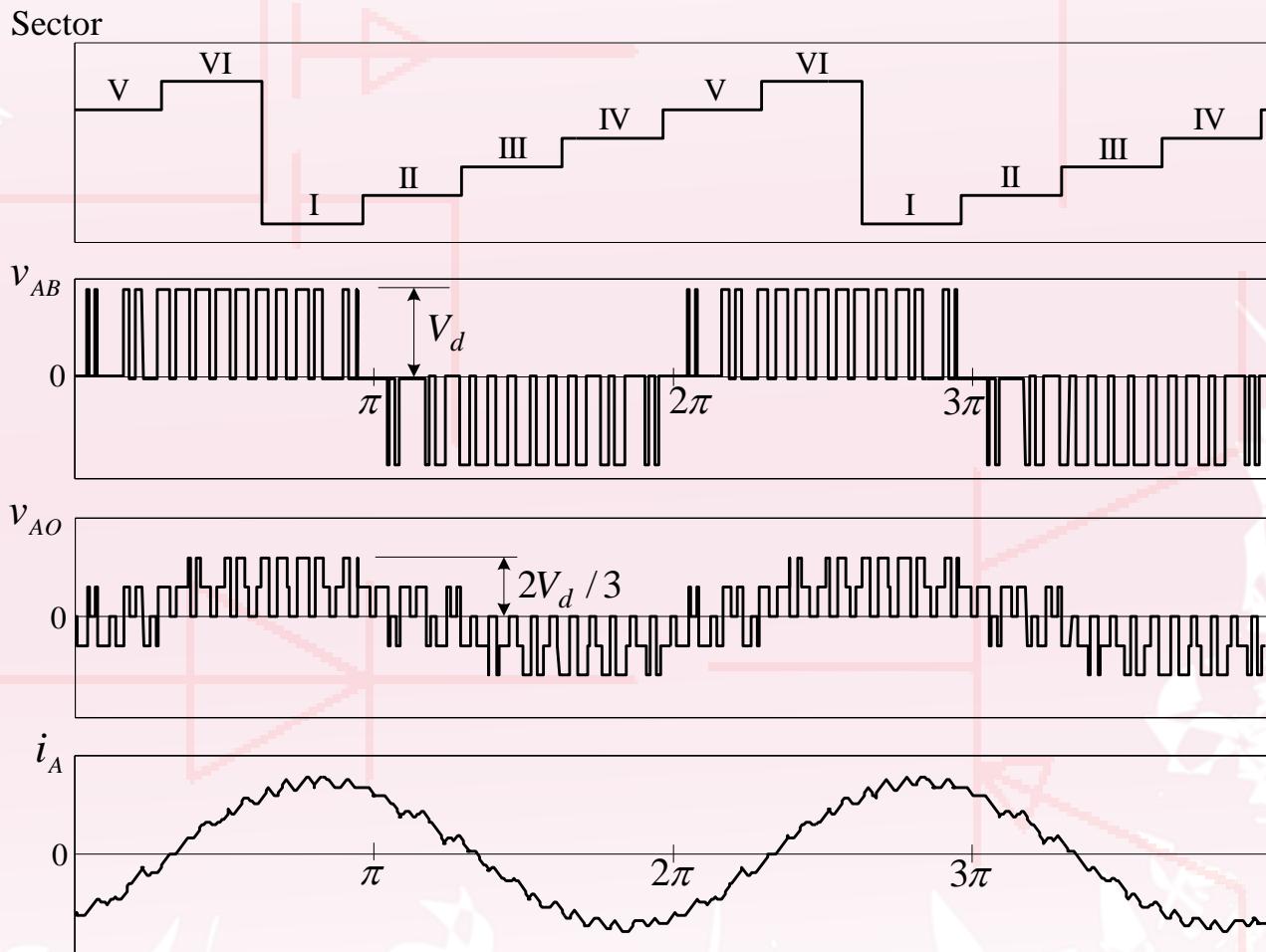


Space Vector Modulation


Waveforms and FFT

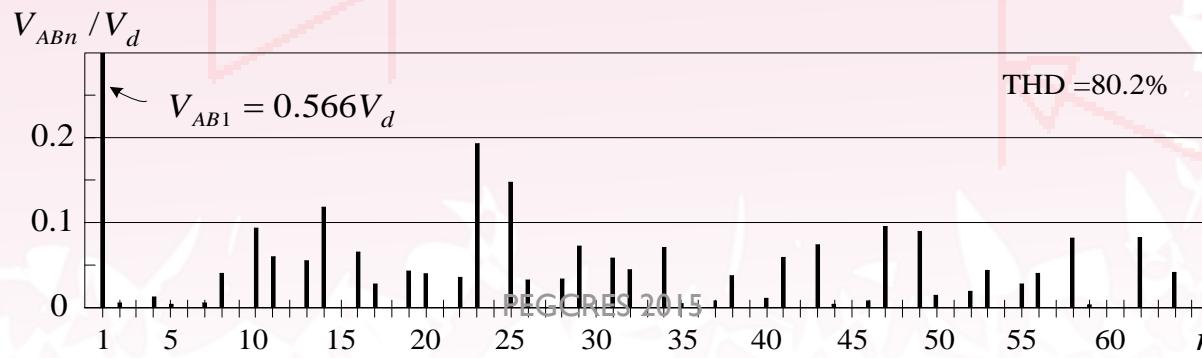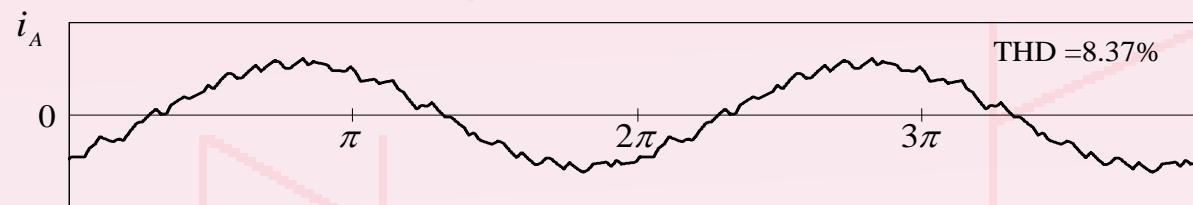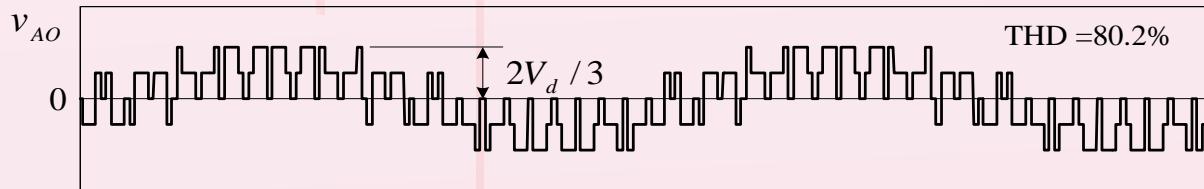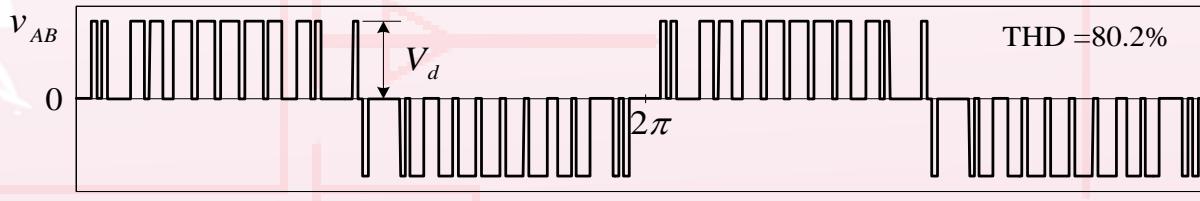

SVPWM – Modified SinePWM

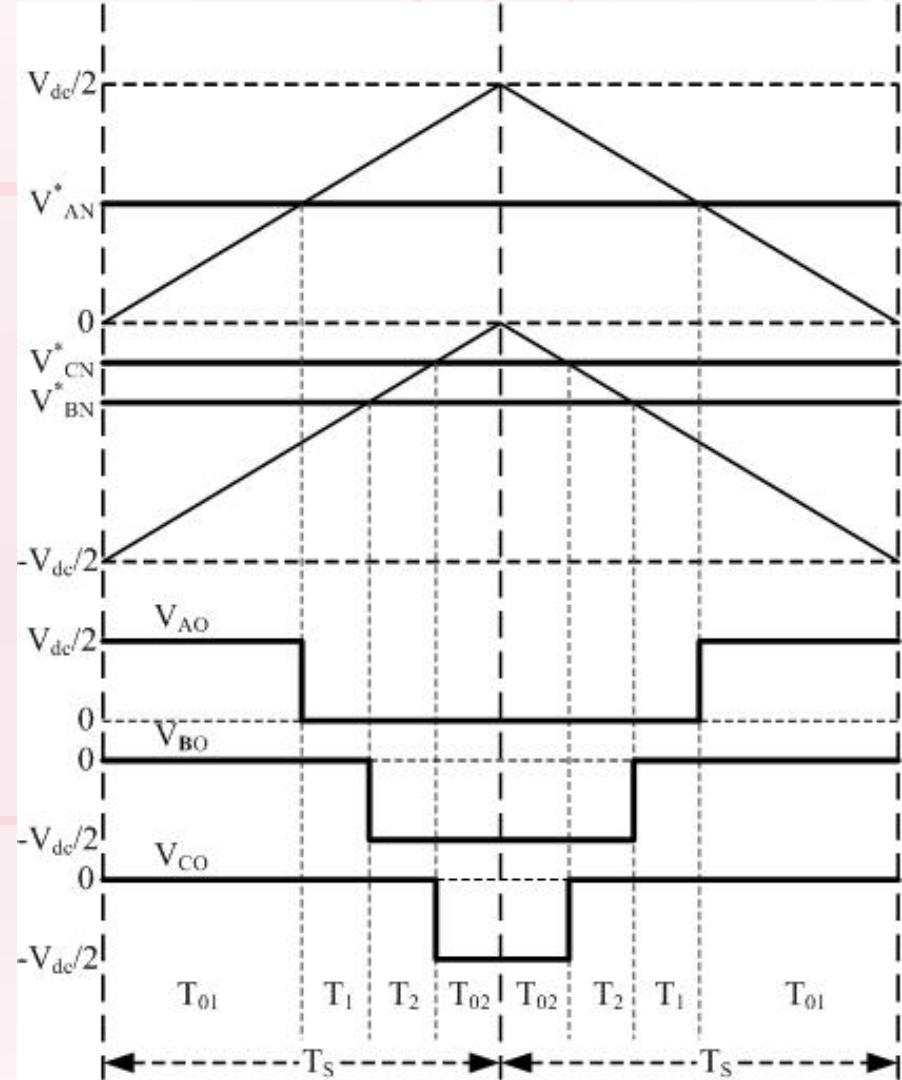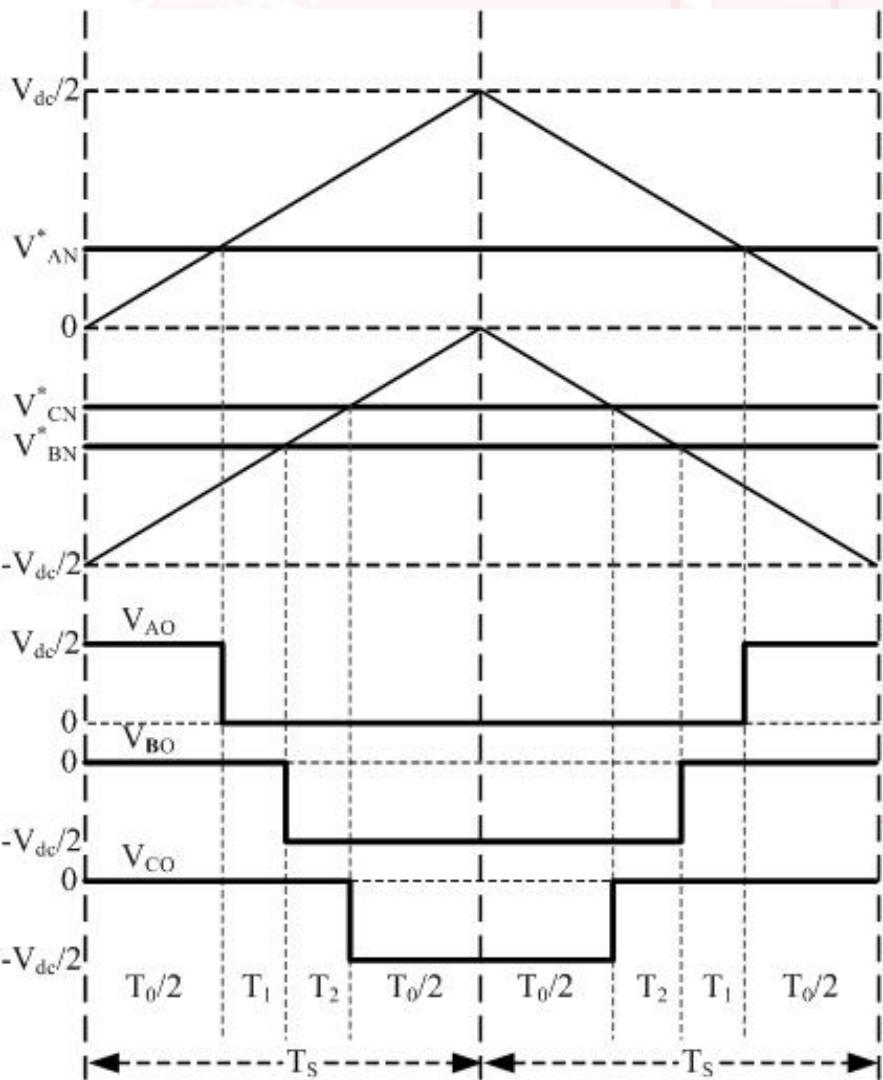

SVPWM – Modified SinePWM

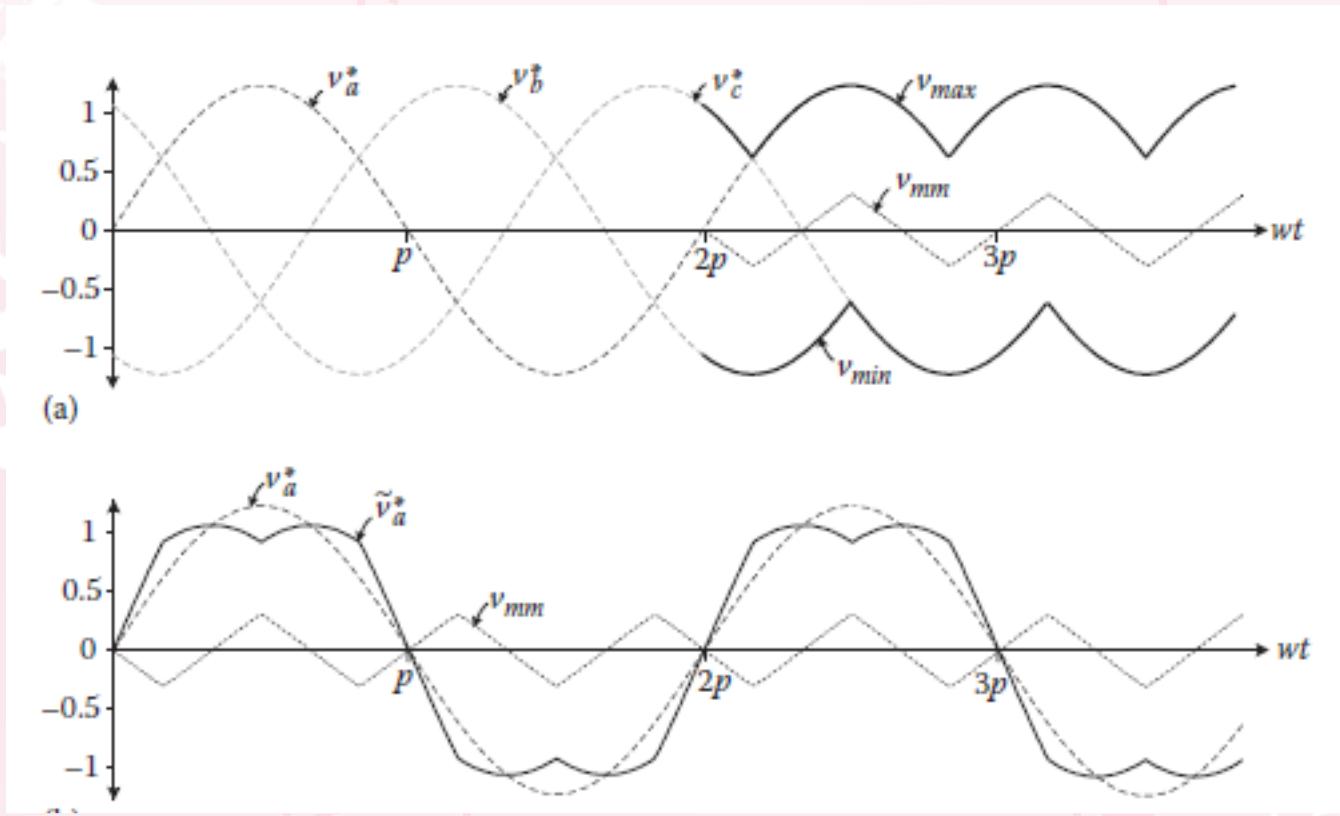

SVPWM – Modified SinePWM

